

— Thevenin and Norton Equivalents


- replace entire circuit, other than two nodes, with a **resistor** and **voltage** source in **series**
- replace entire circuit, other than two nodes, with a **resistor** and **current** source in **parallel**

• Elements


- Open Circuit: $i_{oc} = 0 \rightarrow V_{oc}$
- Short Circuit: $V_{sc} = 0 \rightarrow i_{sc}$

- Ideal Ammeter: short circuit that displays **current**
- Ideal Voltmeter: open circuit that displays **voltage**

• Thevenin (V_{Th} , R_{Th})

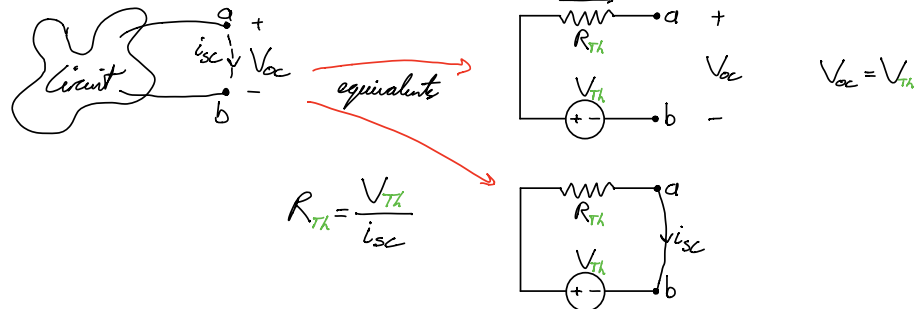

• Norton (I_N , R_N)

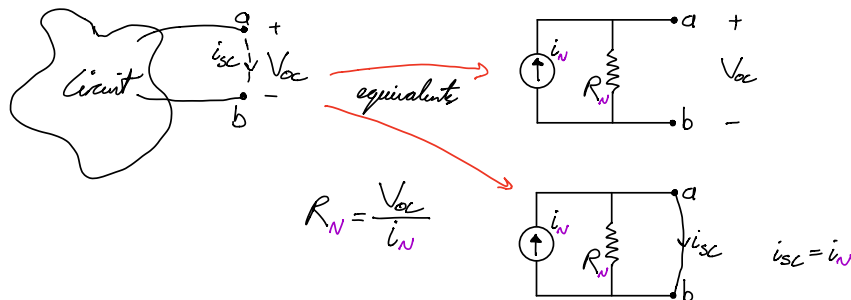

- if all sources are **independent**, kill them and calculate: $R_{eq} = R_{Th}$
- with **dependent** sources, calculate open circuit voltage (V_{oc}), and short circuit current (i_{sc})

P-Operators

- Can represent differential operator by a variable

$$3 \frac{d^2 y}{dt^2} + 5 \frac{dy}{dt} - 8y = 14$$

$$3p^2 y + 5py - 8y = 14 \rightarrow y = \frac{14}{3p^2 + 5p - 8}$$

- Differentiate: $(f(x)=y) \cdot p$
- Integrate: $(f(x)=y) \div p$

- Apply to Inductor: $v = L \frac{di}{dt} = L \cdot pi$
- Apply to Capacitor: $i = C \frac{dv}{dt} \rightarrow v = \frac{1}{C} \cdot \frac{i}{p}$



- Impedance of Elements ($v = Zi$)

$$\text{Capacitor: } Z_C = \frac{1}{Cp}$$

$$\text{Inductor: } Z_L = Lp$$

$$\text{Resistor: } Z_R = R$$

} All Z behave like in Resistors

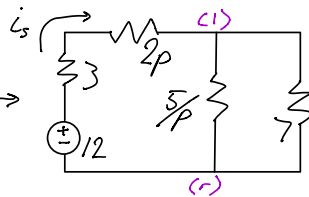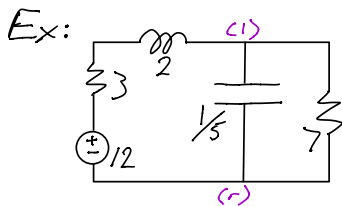

$$K1: \frac{12 - V_1}{3 + 2p} = \frac{V_1 \cdot p}{5} + \frac{V_1}{7}$$

$$\rightarrow V_1 = \frac{420}{14p^2 + 31p + 50}$$

$$i_s = \frac{12 - V_1}{3 + 2p} = \frac{84p + 60}{14p^2 + 31p + 50}$$

$$14p^2 i_s + 31p i_s + 50 i_s = 84p + 60$$


$$14i_s'' + 31i_s' + 50i_s = 60$$

Steady State

- Long term behaviour of circuits and elements

$$C \frac{dv}{dt} = i \quad \text{as } t \rightarrow \infty, \frac{dv}{dt} = 0; \quad i = 0$$
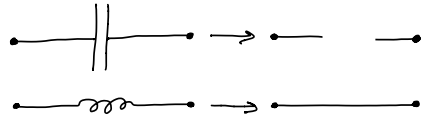
$$L \frac{di}{dt} = v \quad \text{as } t \rightarrow \infty, \frac{di}{dt} = 0; \quad v = 0$$




Energy in Circuit Elements

- Capacitor: $W = \frac{1}{2} CV^2$
- Inductor: $W = \frac{1}{2} Li^2$

Power of a Circuit

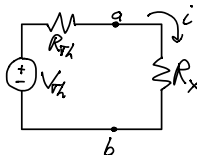- Use Thevenin equivalent to power from a port




$$P_x = R_x \cdot i = \frac{R_x V_{th}^2}{(R_{th} + R_x)^2} \rightarrow \text{power from port a-b}$$

- Maximum power through port

$$\frac{dP_x}{dR_x} = \frac{d}{dR_x} \left(\frac{R_x V_{Th}^2}{(R_{Th} + R_x)^2} \right) = 0 \quad (\text{look for critical points})$$

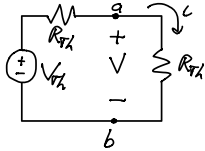
$$R_x = R_{Th} \quad (\text{taking the differential equation})$$



$$\therefore P_{max} = V_i i = \frac{V_{Th}^2}{4R_{Th}}$$

$$i = \frac{V_{Th}}{2R_{Th}}, \quad V = \frac{V_{Th}}{2} \quad (\text{voltage divider})$$

Operational Amplifiers

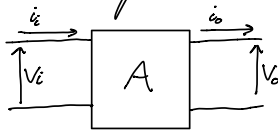

$$A_v = \frac{V_o}{V_i}$$


$$A_v^{dB} = 20 \log_{10} \left| \frac{V_o}{V_i} \right|$$

$$A_i = \frac{i_o}{i_i}$$

$$A_i^{dB} = 20 \log_{10} \left| \frac{i_o}{i_i} \right|$$


$$A_p = \frac{P_o}{P_i}$$

$$A_p^{dB} = 10 \log_{10} \left| \frac{P_o}{P_i} \right|$$

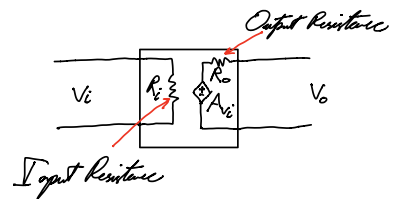


- Difference Amplifier

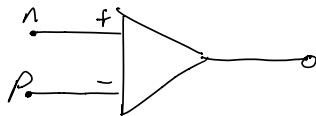- Takes 2 inputs and amplifies the difference



$$A(V_P - V_N)$$

- Op Amp

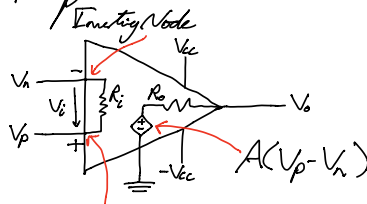


$$R_i = 10^5 \rightarrow 10^{10} \Omega$$

$$R_o = 10 \rightarrow 10^2 \Omega$$

$$A = 10^5 \rightarrow 10^3 \text{ times bigger than } (V_P - V_N)$$

Non-Inverting Node

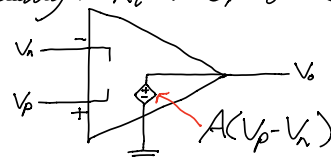- When doing MNA, do not create KCL equation for output node
- Ideally: $R_i \rightarrow \infty, R_o \rightarrow 0, A \rightarrow \infty$



- Saturation



- Output Voltage is bounded by: $-V_{cc} \leq V_o \leq V_{cc}$
- If output voltage reaches extrema, OP Amp becomes saturated

$$V_o = V_{cc} \rightarrow \text{Positive Saturation}$$

$$V_o = -V_{cc} \rightarrow \text{Negative Saturation}$$

Diode

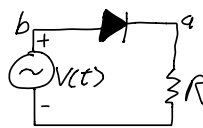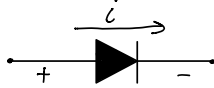- Circuit Element that only allows current in one direction



$$\begin{array}{l} i > 0 \\ v = 0 \end{array} \quad \begin{array}{c} a \\ \text{forward bias} \\ b \end{array}$$

$$\begin{array}{l} v < 0 \\ i = 0 \end{array} \quad \begin{array}{c} a \\ \text{reverse bias} \\ b \end{array}$$

- Current through Real Diode

$$i = I_s \left(e^{\frac{v}{nV_T}} - 1 \right)$$

"-1" can be dropped for approximation

$$V_T = \frac{kT}{q}$$

Boltzmann's Constant

Temperature

Electronic Charge

$\{1 < n < 2\}$ depending on type of Diode

- Iterative Solving Method

- Compute I_s with test case:

$$(V_D, I_D) = (0.7, 0.001)$$


$$(V_D, I_D) = (0.7, 0.001)$$

$$n = 2, V_T = 0.025 \text{ V}$$

$$i = I_s e^{\frac{v}{nV_T}} \rightarrow I_s = \frac{0.001}{\exp\left(\frac{0.7}{2 \cdot 0.025}\right)} = 8.315 \text{ E-10 A}$$

- Two equations:
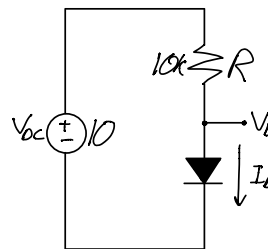
$$I_D = \frac{V_{oc} - V_D}{R} = I_s e^{\frac{V_D}{nV_T}} \quad \text{①} \quad \text{②}$$



- Try a test case for V_D :

$$V_D = 0.7$$

$$\text{① } I_D = \frac{10 - 0.7}{10k} = 930 \mu\text{A}$$

- Now use I_D to compute new V_D

$$I_D = 930 \mu\text{A}$$

$$\text{② } V_D = (2)(0.025) \ln \frac{93 \times 10^{-5}}{8.315 \times 10^{-10}} = 0.6964 \text{ V}$$


Repeat until Diode Voltage stops changing

$$\therefore V_D = 696 \text{ mV}$$

$$I_D = 930 \mu\text{A}$$


- Piecewise Model

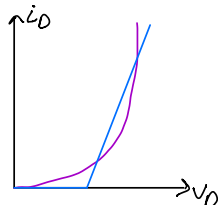- Diode can be simulated with ideal diode, voltage source, and resistor





$$\text{slope} = \frac{1}{r_D}$$

Exponential Characteristic of a Diode

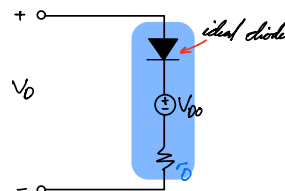

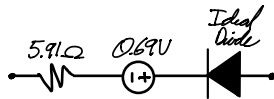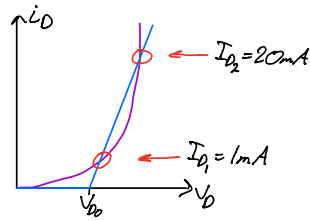Ex: A diode has a voltage drop of $0.7V$ @ $1mA$, $n=1.5$, $V_T=25mV$
Find piecewise model that is exact at $1mA$ & $20mA$



$$I_S = \frac{I_{D1}}{e^{V_{D1}/V_T}} = 7.82 \mu A \quad \text{current source}$$

$$V_{D2} = nV_T \cdot \ln\left(\frac{I_{D2}}{I_S}\right) = 0.81V \quad \text{voltage at } I_{D2}$$

$$\frac{1}{r_D} = \frac{I_{D2} - I_{D1}}{V_{D2} - V_{D1}} \Rightarrow 5.91 \Omega \quad \text{resistance of piecewise model}$$

$$\frac{1}{r_D} = \frac{I_{D1} - 0}{V_{D1} - V_{D0}} \rightarrow V_{D0} = 0.69V \quad \text{voltage when current} = 0$$

• Small Signal Model

- Used when Diode operates with both AC and DC voltages

• DC Steady State:

AC Voltage source $\rightarrow$ short

AC Current source $\rightarrow$ open

Inductor $\rightarrow$ short

Capacitor $\rightarrow$ open

• AC Steady State:

DC Voltage source $\rightarrow$ short

DC Current source $\rightarrow$ open

Inductor $\rightarrow$ open

Capacitor $\rightarrow$ short

• Notations

$\tilde{V}_a \rightarrow$ AC voltage at (a)

$\overline{V}_a \rightarrow$ AC voltage at (a)



$$V_a = \tilde{V}_a + \overline{V}_a$$

Ex:

$$V_D = 0.7V @ 1mA, \quad n=2, \quad V_T = 0.025V$$

$$V_D = \tilde{V}_D + \overline{V}_D$$
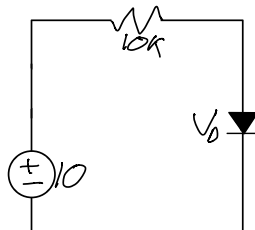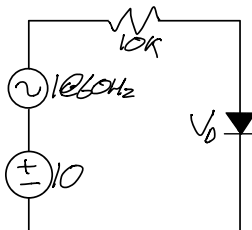
$$I_S = I_D e^{-\frac{V_D}{nV_T}} = 8.32E-10A$$




$$I_D = 0.93mA$$

$$\overline{V}_D = 0.69V$$

$$r_D = \frac{nV_T}{I_D} = 53.8 \Omega$$



DC state

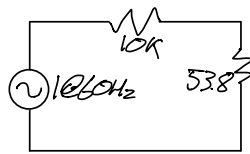


AC State

$$\tilde{V}_D = \frac{1}{10k + 53.8} \cdot 53.8 = 5.35mV$$

$$V_D = 0.69 + 5.35E-3 (\cos(2\pi 60t + \phi)) V$$


• Zener Diodes

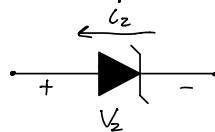- Allows current to flow in reverse direction when voltage across terminals exceeds Zener Voltage




- Can be represented using an incremental model

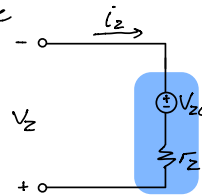r_z is usually found from some test point (V_z, i_z)




$$\Delta V_z = \Delta i_z \cdot r_z$$

$$V_{z0} = V_z - r_z \cdot i_z$$

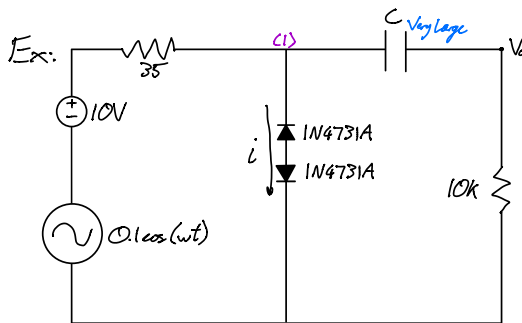


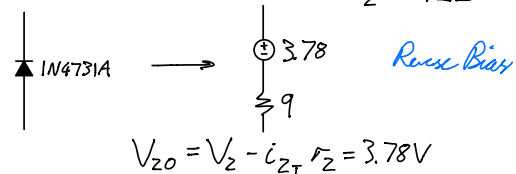From diode table: $(V_z, i_{zT}) = (4.3, 0.058)$
 $r_z = 9\Omega$



$$V_{z0} = V_z - i_{zT} r_z = 3.78V$$

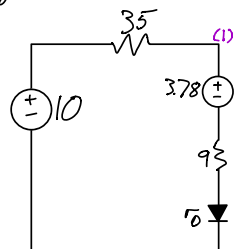For circuit, zener diodes have $(V_F, I_F) = (0.7, 0.8E-3)$ when forward biased; $n=2, V_T=0.025V$




DC State

$$I_s = 0.8E-3 \cdot e^{\frac{-0.7}{0.025}} = 6.65E-10$$

$$e1: I_D = \frac{6.22 - V_D}{44}$$

$$e2: I_D = 6.65E-10 \cdot e^{\frac{V_D}{0.025}} \rightarrow V_D = 0.75V, I_D = 120mA$$
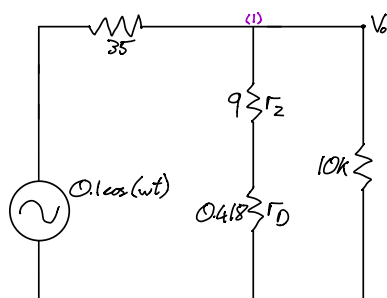
$$r_D = \frac{1}{I_D} \cdot V_T = 0.418\Omega$$




AC State


By Voltage Divider: $V_0 = \frac{0.1\cos(wt)}{44.418} \cdot 9.418$
 $= 0.0213\cos(wt)$

Rectifiers

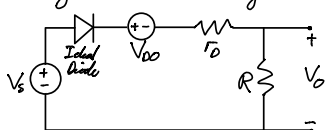- Can be made from Diodes
- Half wave Rectifier



$$V_0(t) = \frac{R}{R + r_D}$$

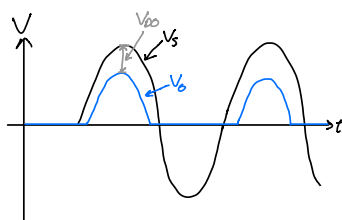

- Peak Inverse Voltage

The PIV is the maximum voltage before diode is at minimum


Ex: for rectifier diode 1N4001, the PIV is 50V and they can dissipate up to 1W

$$I = \frac{1}{50} = 20mA$$

- For Half Wave Rectifier; $PIV = V_s$
- For Full Wave Rectifier; $PIV = 2V_s - V_D$

- Bridge Rectifier



Functions as a full wave rectifier

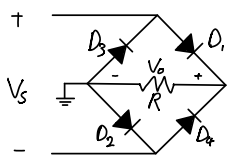

Diodes conduct in pairs: D1 & D2
D3 & D4

$$PIV = V_s - V_D$$

Ripple Voltage

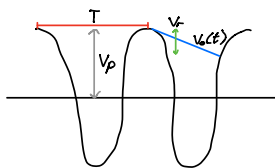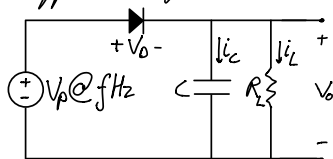

- A decaying exponential resulting from a discharging capacitor: $V_0(t) = V_p \cdot e^{-\frac{t}{RC}}$

After 1 period: $\left\{ \begin{aligned} V_p - V_r &= V_p \cdot e^{-\frac{T}{RC}} \\ e^{-\frac{T}{RC}} &= 1 - \frac{T}{RC} \end{aligned} \right\}$

$$\rightarrow V_r = \frac{V_p - V_0}{f \cdot R_L \cdot C}$$

Half wave rectifier: $f = f$


Full wave rectifier: $f = 2f$

• Load Voltage: $V_{L(ave)} \doteq V_P - \frac{1}{2} V_r$

• Load Current: $i_L \doteq \frac{V_L}{R_L} = \frac{V_o}{R_L} \rightarrow$ if ripple voltage is small: $i_L \doteq \frac{V_o}{R_L}$

Shunt Voltage Regulator

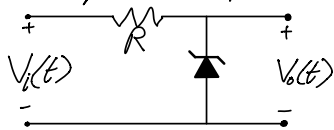• The input and output will have DC and AC components:



$$V_i(t) = \bar{V}_i + \tilde{V}_i(t)$$

$$V_o(t) = \bar{V}_o + \tilde{V}_o(t)$$

$$\bar{V}_o = V_{zo} + \frac{\bar{V}_i - V_{zo}}{R + r_z} \cdot r_z$$

$$\tilde{V}_o(t) = \frac{\tilde{V}_i(t)}{R + r_z} \cdot r_z$$



• In Shunt Regulators, the output is affected by changes in the input voltage: (Line Regulation) and changes in the load current: (Load Regulation)

Line Regulation: $\frac{\Delta V_o}{\Delta V_i} \rightarrow V_o = V_i \cdot \frac{r_z}{r_z + R}$

Load Regulation: $\left| \frac{\Delta V_o}{\Delta i_L} \right| \rightarrow V_o = V_i \cdot \frac{r_z \cdot R}{r_z + R}$

Voltage Limiter

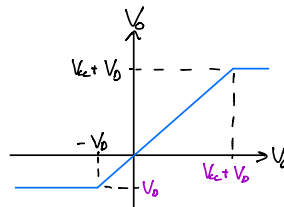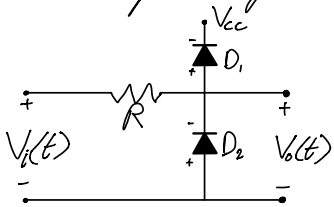• Used to keep an integrated circuit voltage input between specified voltage margins




$$\{-V_o \leq V_o \leq V_{cc} + V_o\}$$

$$V_o = \frac{V_i}{R} \cdot R$$


$$\frac{\Delta V_o}{\Delta V_i} = \frac{R}{R} = 1$$

Bipolar Junction Transistors

• PNP:

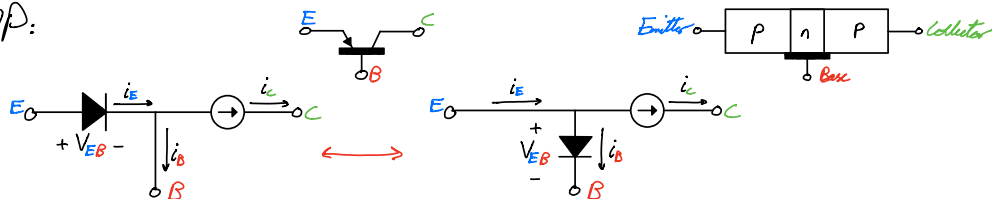

• NPN

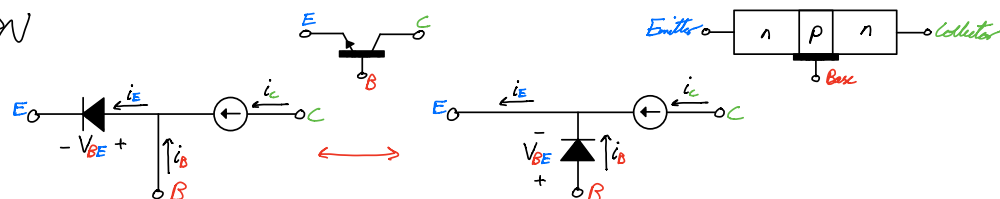

• Relation Equations:



$$i_E = i_C + i_B = i_C \left(1 + \frac{1}{\beta}\right) = i_B (1 + \beta) = \frac{I_s \cdot e^{\frac{V_{BE}}{V_T}}}{\alpha}$$

$$i_C = \alpha \cdot i_E = \beta \cdot i_B = I_s \cdot e^{\frac{V_{BE}}{V_T}}$$

$$i_B = \frac{I_s \cdot e^{\frac{V_{BE}}{V_T}}}{\beta}$$

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$

Ex: Calculate V_{BE} and i_C @ 293K

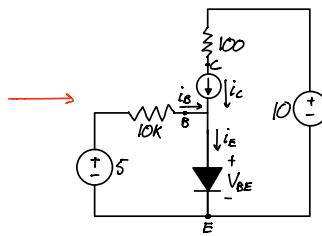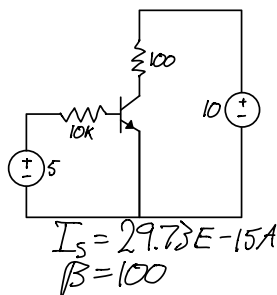

$$V_B = V_{BE} + 0$$

$$0 = 5 - i_B \cdot 10k - V_{BE}$$

$$5 = \frac{I_s}{\beta} \cdot e^{\frac{V_{BE}}{V_T}} + V_{BE}$$

$$V_{BE} = 0.7V$$

$$i_C = 43mA$$

• BJT Modes of Operation


	EB Junction	CB Junction	i_C
Cutoff — Open Switch	Reverse Biased	Reverse Biased	$= 0$
Active — Amplifier	Forward Biased	Reverse Biased	$= \beta \cdot i_B$
Saturation — Closed Switch	Forward Biased	Forward Biased	$< \beta \cdot i_B$

• DC BJT Circuit


• Represent Diode from BJT with a Voltage Source

Ex: Voltage Regulator from a BJT and Zener Diode

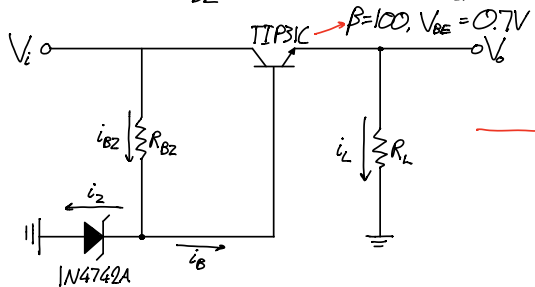Calculate R_{BZ} when $V_i = 15V$, $i_L = 1A$



$$V_Z = 12V @ 2mA, r_z = 9\Omega$$

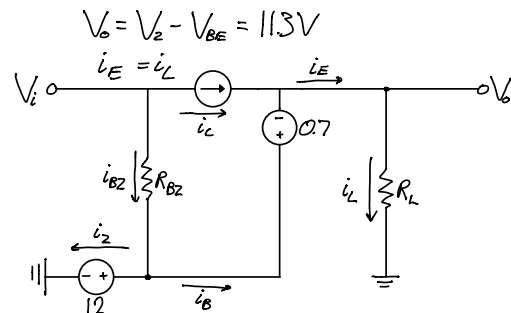


$$R_L = \frac{V_o}{i_L} = 11.3\Omega$$

$$R_{BZ} = \frac{V_i - V_Z}{i_{BZ}} = 97\Omega$$

$$i_B = \frac{i_C}{\beta} = \frac{\alpha \cdot i_E}{\beta} = 9.9mA$$

$$i_{BZ} = i_B + i_Z = 30.9mA$$

Ex: Find i_B, i_C, i_E, V_{CE}

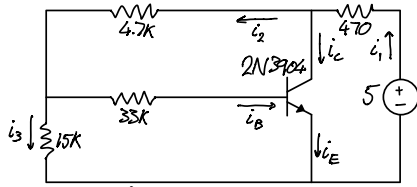


$$\beta = 100$$

$$i_B = 42 \mu A$$

$$i_C = 4.20 mA$$

$$i_E = 4.24 mA$$

$$V_{CE} = 2.94 V$$

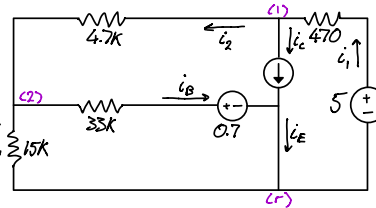

$$K1: \frac{5 - V_1}{4.7k} = i_C + \frac{V_1 - V_2}{4.7k}$$

$$i_B = \frac{V_2 - 0.7}{33k}$$

$$K2: \frac{V_1 - V_2}{4.7k} = \frac{V_2 - 0.7}{33k} + \frac{V_2}{15k}$$




$$i_C = 100 \cdot i_B$$

$$V_{CE} = V_1 - V_2$$

$$i_E = 101 \cdot i_B$$


• BJT Amplifiers

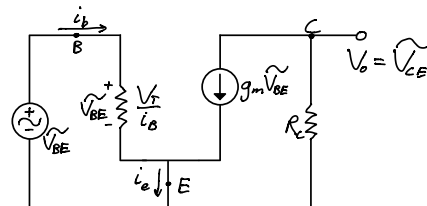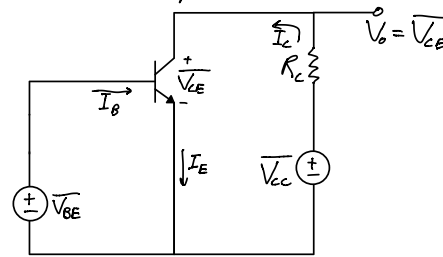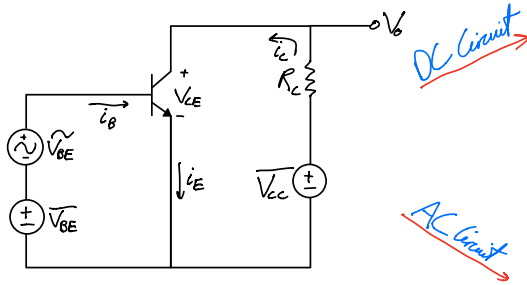- Separate amplifier circuit into AC and DC components:



- This AC circuit model fits the small signal AC equivalent of the Amplifier
- Solving BJT Amplifiers
 - 1) Solve DC circuit for $I_C, r_{\pi}/r_e, g_m$
 - 2) Solve AC circuit (Hybrid- π or T model) for $A_v = \frac{V_o}{V_i}$

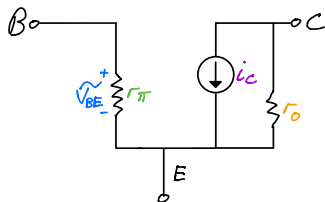• Hybrid- π Circuit (AC Small Signal Equivalent)




$$i_c = g_m \cdot \tilde{V}_{BE} = \frac{I_C}{V_T} \tilde{V}_{BE} = \frac{i_s \cdot e^{\frac{\tilde{V}_{BE}}{V_T}}}{V_T} \tilde{V}_{BE} = i_b \cdot \beta$$

$$r_{\pi} = \frac{\tilde{V}_{BE}}{i_b} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

NPN: $i_c, \tilde{V}_{BE}$ PNP: $-i_c, -\tilde{V}_{BE}$

$r_o = \frac{V_A}{I_C}$, where V_A is V_{CE} when $i_c = 0$

- T circuit (AC Small Signal Equivalent)

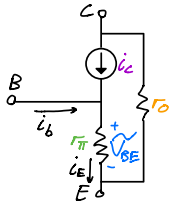

$$i_c = g_m \cdot \tilde{v}_{BE} = \frac{I_c}{V_T} \tilde{v}_{BE} = \frac{i_s \cdot e^{\frac{\tilde{v}_{BE}}{V_T}}}{V_T} \tilde{v}_{BE}$$


$$r_{\pi} = \frac{\alpha}{g_m} = \frac{V_T}{I_E}$$

$$r_o = \frac{V_A}{I_c}, \text{ where } V_A \text{ is } V_{CE} \text{ when } i_c = 0$$

- Common Emitter Amplifier

- In AC, the **Emitter** is connected to ground


Ex: Find $A_v = \frac{V_o}{V_s}$, V_c

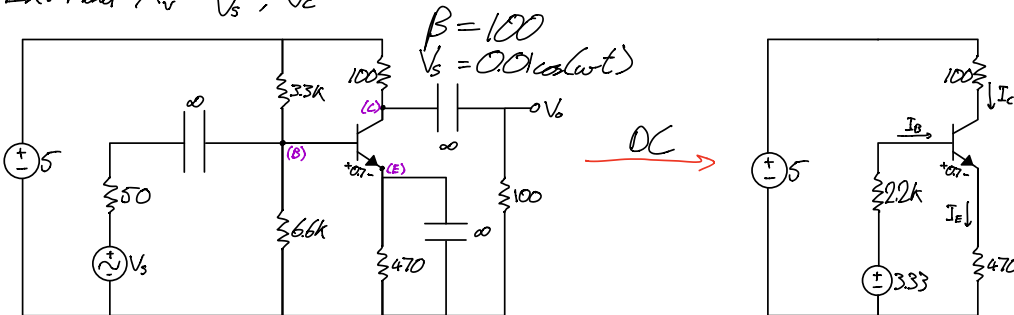

AC

$$3.33 = 2.2k \cdot I_B + 0.7 + (\beta + 1) \cdot I_B \cdot 470$$
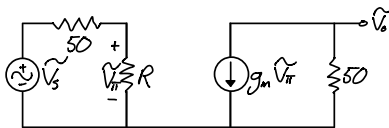
$$I_c = \beta \cdot I_B = 5.302 \text{ mA}$$



$$r_{\pi} = \beta \cdot \frac{I_c}{I_E} = 100 \cdot \frac{5.302 \text{ E-}3}{25 \text{ E-}3} = 476 \Omega$$

$$R = (3.3k \parallel 6.6k \parallel 476) = 392 \Omega$$

$$g_m V_{\pi} = \frac{I_c}{V_T} \cdot V_{\pi} = 0.21 V_{\pi} \text{ A}$$

$$V_{\pi} = \frac{V_s}{50 + 392} \cdot 392$$

$$V_o = -0.21 \cdot V_{\pi} \cdot 50$$

$$V_s = \frac{V_{\pi}}{0.887}$$

$$A_v = \frac{V_o}{V_s} = -9.134$$

- Common Emitter Amplifier with Resistance in Emitter

- In AC, the **Emitter** is connected to a **resistance** and then ground


- Common Base Amplifier

- In AC, the **Base** is connected to ground

• BJT Switch — Saturation Operation

- BJTs can operate in **cut-off**, **saturation** and **active** modes

Ex:

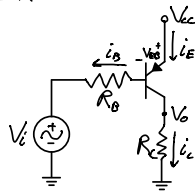

$$V_{CC} = i_B R_B + V_{EB} + V_i$$


if: $V_i = V_{CC} \rightarrow i_B = 0 \rightarrow \text{cutoff}$

$V_i < (V_{CC} - V_{EB}) \rightarrow i_B = \frac{V_{CC} - V_{EB}}{R_B} \rightarrow \text{active}$
 $V_o = i_C R_C$


$V_{EC} < V_{EC(sat)}$ $\rightarrow$ **saturation**
 $V_o = V_{CC} - V_{EC(sat)}$

- A transistor operates as a switch in either **cut-off** or **saturation** modes
- In **cut-off**; transistor becomes open circuit
- In **saturation**; transistor becomes:

NPN

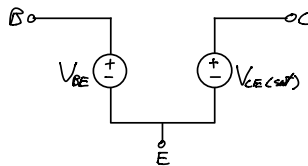


PNP

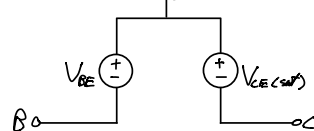

• Current Mirror



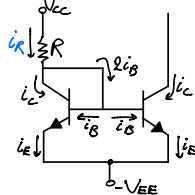
- "Copies" current through one active device to another




$$i_C = i_R \cdot \frac{\beta}{\beta + 2}$$

Mosfet

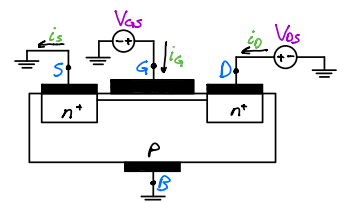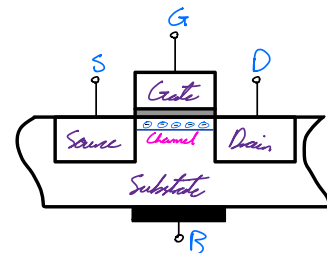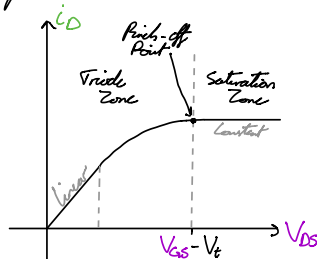- When a large enough **gate** voltage is reached, the current will flow between the **source** and **drain**
- To create this **channel**, V_{GS} must be atleast the Threshold Voltage (V_t)



- NFET

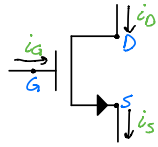


- Cutoff Region: $i_D = i_S = 0$, $V_{GS} < V_t$

- Triode Region: $i_D = i_S = K_n' \cdot \frac{W}{L} \cdot \left[(V_{GS} - V_t) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right] = \frac{V_{DS}}{r_{DS}}$
 $r_{DS} = \left[\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t) \right]^{-1}$, $0 < V_{DS} < V_{GS} - V_t$

- Saturation Region: $i_D = i_S = \frac{1}{2} K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A} \right)$, $V_{DS} \geq V_{GS} - V_t$

- PFET

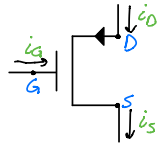



- Cutoff Region: $i_D = i_S = 0$, $|V_{GS}| < |V_t|$

- Triode Region: $i_D = i_S = K_p' \cdot \frac{W}{L} \cdot \left[|V_{GS} - V_t| \cdot |V_{DS}| - \frac{|V_{DS}|^2}{2} \right] = \frac{V_{DS}}{r_{DS}}$
 $r_{DS} = \left[\mu_p C_{ox} \frac{W}{L} (V_{GS} - V_t) \right]^{-1}$, $0 < |V_{DS}| < |V_{GS} - V_t|$


- Saturation Region: $i_D = i_S = \frac{1}{2} K_p' \cdot \frac{W}{L} \cdot (V_{GS} - V_t)^2 \left(1 + \frac{|V_{DS}|}{|V_A|} \right)$, $|V_{DS}| \geq |V_{GS} - V_t|$

- Depletion MOSFET

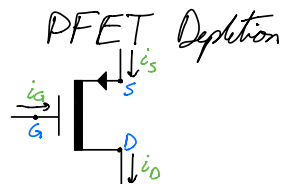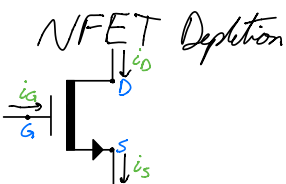- Current between drain and source regardless of voltage at gate



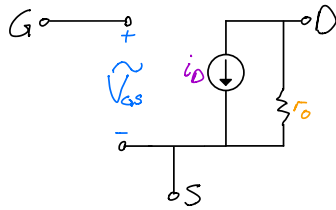
- Hybrid- π Circuit (AC Small Signal Equivalent)



$$i_D = g_m \cdot \tilde{V}_{GS} = K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t) \cdot \tilde{V}_{GS}$$

$$r_O = |V_A| \cdot \left[\frac{1}{2} K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t)^2 \right]^{-1} = \frac{|V_A|}{I_D}$$

- T Circuit (AC Small Signal Equivalent)

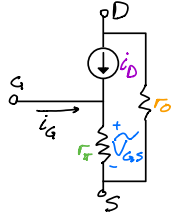


$$i_D = g_m \cdot \tilde{V}_{GS} = K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t) \cdot \tilde{V}_{GS}$$

$$r_O = |V_A| \cdot \left[\frac{1}{2} K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t)^2 \right]^{-1} = \frac{|V_A|}{I_D}$$

$$r_{\pi} = \frac{1}{g_m} = \left[K_n' \cdot \frac{W}{L} \cdot (V_{GS} - V_t) \right]^{-1}$$

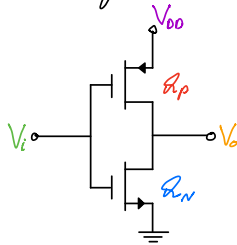- Mosfets can be used in various amplifier circuits
- Complementary Mosfet (CMOS) Logic Inverter
 - An NFET and PFET where one is in cut-off, and the other is in Triode
 - This arrangement makes $V_o = 0$ if $V_i = V_{DD}$, and $V_o = V_{DD}$ if $V_i = 0$




- When $V_i = V_{DD}$: $V_{GS} = 0V \rightarrow$ cutoff

$$i_s = i_D = K_n' \cdot \frac{W}{L} \cdot \left[(V_{DD} - V_t) \cdot V_o - \frac{V_o^2}{2} \right]$$

Can approximate NFET to linear resistance:
Simplifying the circuit to:
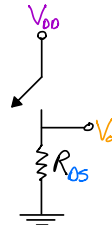
$$R_{DS} = \left[K_n' \cdot \frac{W}{L} (V_{DD} - V_t) \right]^{-1}$$




• When $V_i = 0$:


$V_{GS} = 0V \rightarrow \text{cutoff}$

$$i_S = i_D = K_p' \cdot \frac{W}{L} \cdot \left[(|V_{DD}| - |V_t|) \cdot |V_o - V_{DD}| - \frac{(V_o - V_{DD})^2}{2} \right]$$

Can approximate PFET to linear resistance: $R_{DS} = \left[K_p' \cdot \frac{W}{L} (V_{DD} - |V_t|) \right]^{-1}$
Simplifying the circuit to:

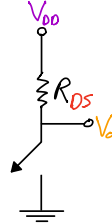

• NMOS Switches

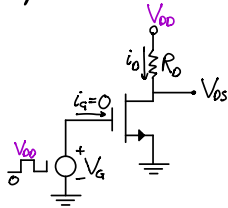

V_G can be V_{DD} (Triode Mode) or 0 (Cut-off mode)

Can approximate NFET to linear resistance:

$$R_{DS} = \frac{V_{DS}}{I_D} = \left[K_n' \cdot \frac{W}{L} (V_{GS} - V_t) \right]^{-1}$$

Simplifying the circuit to:

